 


## HW3

1. Fix the hazard that may occur in the following figures:



2. Design a combinational circuit with three inputs,  $x$  (MSB),  $y$ , and  $z$  (LSB), and three outputs,  $A$  (MSB),  $B$ , and  $C$  (LSB). When the binary input is 0, 1, or 2, the binary output is three greater than the input ( $xyz=001$  (1)  $\Rightarrow ABC=100$  (4),  $xyz=010$  (2)  $\Rightarrow ABC=101$  (5)). When the binary input is 3, 4, 5, 6, or 7, the binary is two less than the input ( $xyz=110$  (6)  $\Rightarrow ABC=100$  (4),  $xyz=100$  (4)  $\Rightarrow ABC=010$  (2)).
  - (a) Derive the truth table.
  - (b) Derive the simplified Boolean expressions for  $A$ ,  $B$ , and  $C$  using maps.
  - (c) Draw the related logic diagram.
3. Design an excess-3-to-binary decoder using the unused combinations of the code as don't-care conditions.
4. Simplify the following Boolean expressions to a minimum number of literals, and implement with two-level NAND-NAND, NOR-NOR, AND-OR-Invert, and OR-AND-Invert gates, respectively.
  - (a)  $xy'z + xy'z' + xyz'$ ,
  - (b)  $(y'z + xw')(xw + y'z)$ .
5. A half adder is a circuit that takes in one-bit binary numbers  $a$  and  $b$ , and outputs a sum  $s$  and a carry out  $co$ . The concatenation of  $co$  and  $s$ , is the two-bit value that results from adding  $a$  and  $b$  (e.g. if  $a=1$ ,  $b=1$ ,  $s=0$ , and  $co=1$ ).
  - (a) Derive the truth table of a half adder.
  - (b) Derive the Boolean expression of  $co$  and  $s$  in the simplest sum-of-product form.
  - (c) Find the prime implicants and essential prime implicants of  $co$  and  $s$ .
6. Use Verilog to simulate the half adder in problem 5.

